

S1 – Examination 2

Computer Architecture

Duration: 1 hr 30 min.

Family name: First name: Class:

Answer on the worksheet.

Do not show any calculation unless you are explicitly asked.

Do not use a pencil or red ink.

Exercise 1 (5 points)

Simplify the expressions below as much as possible. The result must not contain parentheses.

Non-simplified expression	Most simplified expression (no parentheses)
$\overline{(C + D)} + (B + \overline{D})$	
$(B + \overline{D}).(\overline{A} + \overline{D}).(A + D).A.B$	
$\overline{A.B.C.D} + \overline{A.B.C.D} + \overline{A.B.C.D} + \overline{A.B.C.D}$	
$\overline{A.B}.(A.B + C) + A.B.C$	
$(B + \overline{D} + C.B).\overline{\overline{C.B.C.B}}$	

Exercise 2 (4 points)

1. Write down the minterm canonical form for the following expressions.

Expression	Minterm canonical form
$A.B.C + A.\overline{B}$	
$(\overline{A} + \overline{C}).(A + C + \overline{D}).B.\overline{C}$	

2. Write down the maxterm canonical form for the following expressions.

Expression	Maxterm canonical form
$(A + C).(\overline{A} + B + C)$	
$A+B.C$	

Exercise 3 (6 points)

Complete the Karnaugh maps below (**circles included**) and give their most simplified expressions. **No points will be given to an expression if its Karnaugh map is wrong.**

3. Let us consider N , a 3-bit binary number (C, B, A). A is the least significant bit.

- $S1 = 1$ when $N = 1, 3, 4, 5$
- $S2 = 1$ when $N = 0, 2, 4, 5, 6, 7$

		BA			
	S1	00	01	11	10
C	0				
	1				

S1 =

		BA			
	S2	00	01	11	10
C	0				
	1				

S2 =

4. Let us consider N , a 4-bit binary number (D, C, B, A). A is the least significant bit.

- $S3 = 1$ when $N = 0, 1, 2, 3, 4, 5, 6, 7, 9, 11, 13, 15$
- $S4 = 1$ when $N = 0, 1, 4, 6, 8, 9, 12, 14$
- $S5 = 1$ when $N = 0, 2, 8, 10$ and $S5$ is undefined when $N = 5, 7, 13, 15$
- $S6 = 1$ when $N = 2, 6$ and $S6$ is undefined when $N = 0, 1, 4, 5, 8, 9, 12, 13$

		BA			
	S3	00	01	11	10
DC	00				
	01				
	11				
	10				

S3 =

		BA			
	S4	00	01	11	10
DC	00				
	01				
	11				
	10				

S4 =

		BA			
	S5	00	01	11	10
DC	00				
	01				
	11				
	10				

S5 =

		BA			
	S6	00	01	11	10
DC	00				
	01				
	11				
	10				

S6 =

Exercise 4 (3 points)

Four managers at a company (A, B, C and D) can have access to a safe. They each have a different key. It has been decided that:

- A can only open the safe if at least one of the B or C managers is present.
- B, C and D can only open it if at least two of the other managers are present.

1. In the truth table below, we consider that:

- A = 0 means that A is absent (same for B, C and D).
- A = 1 means that A is present (same for B, C and D).
- S = 0 means that the safe cannot be opened.
- S = 1 means that the safe can be opened.

Complete the truth table.

A	B	C	D	S
0	0	0	0	
0	0	0	1	
0	0	1	0	
0	0	1	1	
0	1	0	0	
0	1	0	1	
0	1	1	0	
0	1	1	1	
1	0	0	0	
1	0	0	1	
1	0	1	0	
1	0	1	1	
1	1	0	0	
1	1	0	1	
1	1	1	0	
1	1	1	1	

2. Give the most simplified expression for S (the result must be given without parentheses).

S =

Exercise 5 (2 points)

We want to design a 1-bit comparator with the following inputs and outputs:

- Inputs: two bits to compare (A and B).
- Outputs: ' $A > B$ ', ' $A = B$ ' and ' $A < B$ ' with:
 - ' $A > B$ ' = 1 if and only if $A > B$.
 - ' $A = B$ ' = 1 if and only if $A = B$.
 - ' $A < B$ ' = 1 if and only if $A < B$.

1. Complete the following truth table.

A	B	'A > B'	'A = B'	'A < B'

2. Give the most simplified expression for the outputs. **If possible, you must use the EXCLUSIF OR operator.**

'A > B' =	'A = B' =	'A < B' =
---------------------	------------------	---------------------

Feel free to use the blank space below if you need to: