

# Final Exam S2

## Computer Architecture

Duration: 1 hr 30 min.

Answer on the answer sheet only.

Do not show any calculation unless you are explicitly asked.

Do not use red ink.

### **Exercise 1 (5 points)**

1. Convert the numbers given on the answer sheet into their **single-precision** IEEE-754 representations. Write down the final result in its **binary form** and specify the three fields.
2. Convert the **double-precision** IEEE-754 words given on the answer sheet into their associated representations. If a representation is a number, use the following base-10 form:  $k \times 2^n$  where  $k$  and  $n$  are integers (either positive or negative).

### **Exercise 2 (4 points)**

We want to build a 2-Mib ROM device (labelled  $M$ ) from several 16-Kib ROM devices (labelled  $m$ ). The  $M$  device has a 16-bit data bus. The  $m$  devices have a 4-bit data bus. Answer the questions on the answer sheet.

### **Exercise 3 (5 points)**

1. Wire the flip-flops (figure 1) in order to design a **modulo-11 asynchronous up counter**.
2. Wire the flip-flops (figure 2) in order to design a **modulo-11 asynchronous down counter**.
3. Wire the flip-flops (figure 3) in order to design a **shift register** ( $E \rightarrow Q0 \rightarrow Q1 \rightarrow Q2 \rightarrow Q3$ ).

### **Exercise 4 (6 points)**

The table shown on the answer sheet gives the sequence of a counter we want to design. This counter should be made up of JK flip-flops.

1. Complete the table shown on the answer sheet.
2. Write down the most simplified expressions of  $J$  and  $K$  for each flip-flop on the answer sheet. **Complete the Karnaugh maps for the solutions that are not obvious**. An obvious solution does not have any logical operations apart from the complement (for instance:  $J0 = 1$ ,  $K1 = \overline{Q2}$ ).



Last name: ..... First name: ..... Group: .....

**ANSWER SHEET**

**Exercise 1**

1.

Number	S	E	M
75.75			
0.46875			

2.

IEEE-754 Representation	Associated Representation
20A1 8000 0000 0000 <sub>16</sub>	
7FF7 0000 0000 0000 <sub>16</sub>	
0004 2000 0000 0000 <sub>16</sub>	

**Exercise 2**

Question	Answer
What is the depth of the <i>m</i> memory?	
What is the depth of the <i>M</i> memory?	
What is the number of address lines of the <i>m</i> memory?	
What is the number of address lines of the <i>M</i> memory?	
How many memory devices should be put in parallel?	
How many memory devices should be put in series?	
How many address lines are required to control the <i>CS</i> input of the memory devices?	
When the <i>M</i> memory is active, how many <i>m</i> memory devices are active simultaneously?	

**Exercise 3**

 


Figure 1

 


Figure 2

 


Figure 3

**Exercise 4**

Q2	Q1	Q0	J2	K2	J1	K1	J0	K0
0	0	0						
0	0	1						
0	1	1						
0	1	0						
1	1	0						
1	1	1						
1	0	1						
1	0	0						

**Do not use Karnaugh maps for obvious solutions.**

		Q1 Q0				
		J0	00	01	11	10
Q2	0					
	1					

J0 =

		Q1 Q0				
		K0	00	01	11	10
Q2	0					
	1					

K0 =

		Q1 Q0				
		J1	00	01	11	10
Q2	0					
	1					

J1 =

		Q1 Q0				
		K1	00	01	11	10
Q2	0					
	1					

K1 =


		Q1 Q0				
		J2	00	01	11	10
Q2	0					
	1					

J2 =

		Q1 Q0				
		K2	00	01	11	10
Q2	0					
	1					

K2 =

Feel free to use the blank space below if you need to:

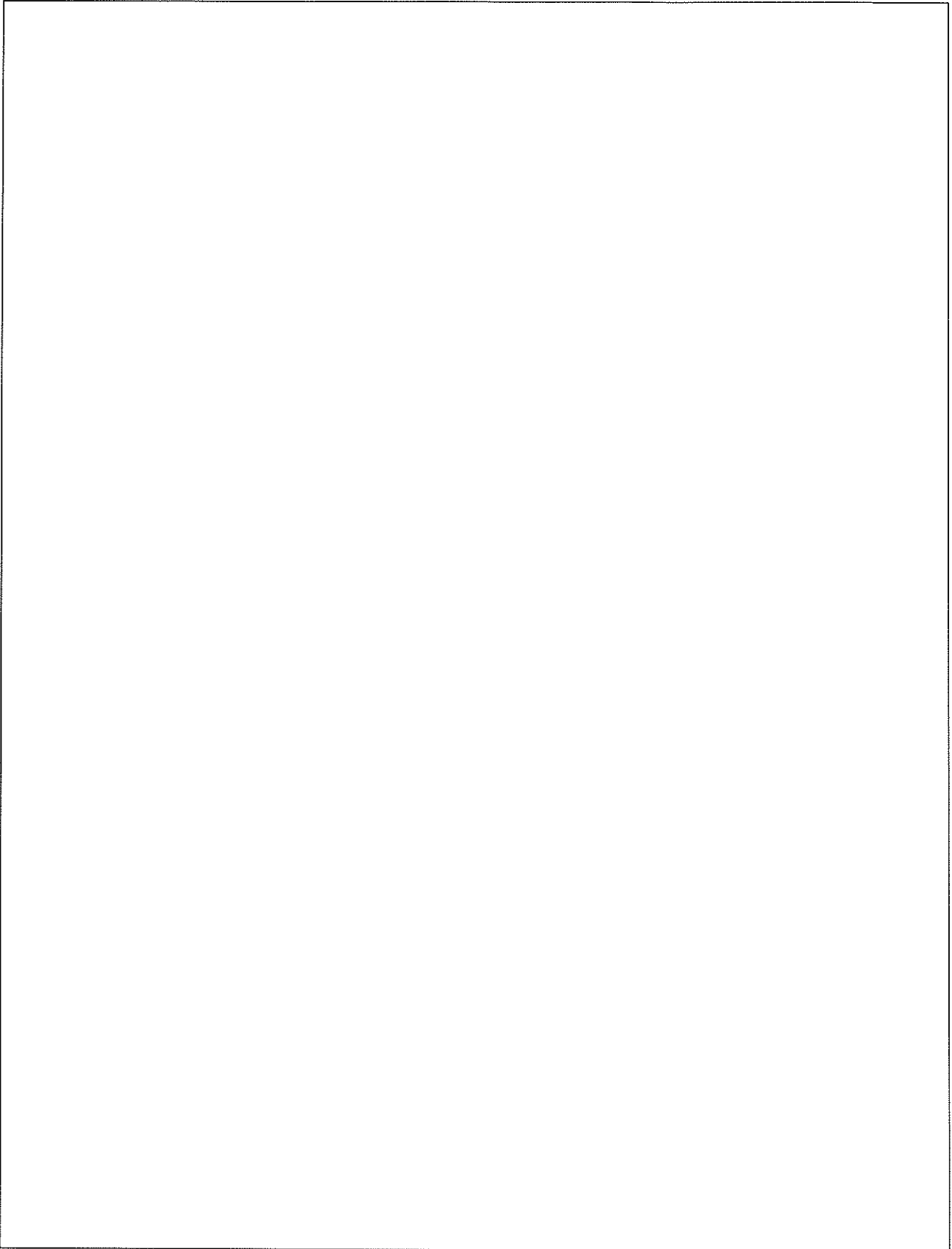A large, empty rectangular box with a thin black border, occupying most of the page. It is intended for the student to write their answers to the exam questions.