

Key to Final Exam S2

Computer Architecture

Duration: 1 hr 30 min

Answer on the answer sheet only.

Do not show any calculation unless you are explicitly asked.

Do not use red ink.

Exercise 1 (5 points)


- Convert the numbers given on the [answer sheet](#) into their **single-precision** IEEE-754 representations. Write down the final result in its **binary form** and specify the three fields.
- Convert the **double-precision** IEEE-754 words given on the [answer sheet](#) into their associated representations. If a representation is a number, use the base-10 following form: $k \times 2^n$ where k and n are integers (either positive or negative).

Exercise 2 (5 points)

Answer the questions on the [answer sheet](#).

 Exercise 3 (5 points)

- Wire the flip-flops ([figure 1](#)) in order to design a **modulo-14 asynchronous up counter**.
- Wire the flip-flops ([figure 2](#)) in order to design a **modulo-14 asynchronous down counter**.
- Complete the timing diagrams shown on the [answer sheet](#) (up to the last vertical dotted line) for the following circuit.



Exercise 4 (6 points)

The table shown on the [answer sheet](#) gives the sequence of a counter we want to design. This counter should be made up of JK flip-flops.

- Complete the table shown on the [answer sheet](#).
- Write down the most simplified expressions of J and K for each flip-flop on the [answer sheet](#). **Complete the Karnaugh maps for the solutions that are not obvious.** An obvious solution does not have any logical operations apart from the complement (for instance: $J_0 = 1$, $K_1 = \overline{Q_2}$).

Last name: First name: Group:

ANSWER SHEET

Exercise 1

1.

Number	S	E	M
217.25	0	10000110	101100101000000000000000
0.21875	0	01111100	110000000000000000000000

2.

IEEE-754 Representation	Associated Representation
423E 0000 0000 0000 ₁₆	15×2^{33}
8003 8000 0000 0000 ₁₆	-7×2^{-1027}
7FF0 0000 0000 0000 ₁₆	$+\infty$

Exercise 2

Question	Answer
A memory has a depth of 64 Ki words. How many address lines does this memory have?	16 lines
A memory has an 8-bit data bus and a 16-bit address bus. In a power of two, what is the capacity in bits of this memory?	2^{19} bits
An M1 memory has a 16-bit data bus and a 32-bit address bus. Two M1 memories are connected in series to build an M2 memory. What is the size of the address bus of the M2 memory?	33 bits
A microprocessor has a 20-bit address bus. Three address lines are used for selecting the devices. With the linear address decoding, what is the maximum number of address lines that a device connected to this microprocessor can have?	17 lines
A microprocessor has a 24-bit address bus. Using the linear address decoding, we connect this microprocessor to the following devices. <ul style="list-style-type: none"> • a ROM device (20 address lines) • a RAM device (15 address lines) • a peripheral device (10 address lines) How many bits are unused in the case of the RAM device?	6 bits

Exercise 3

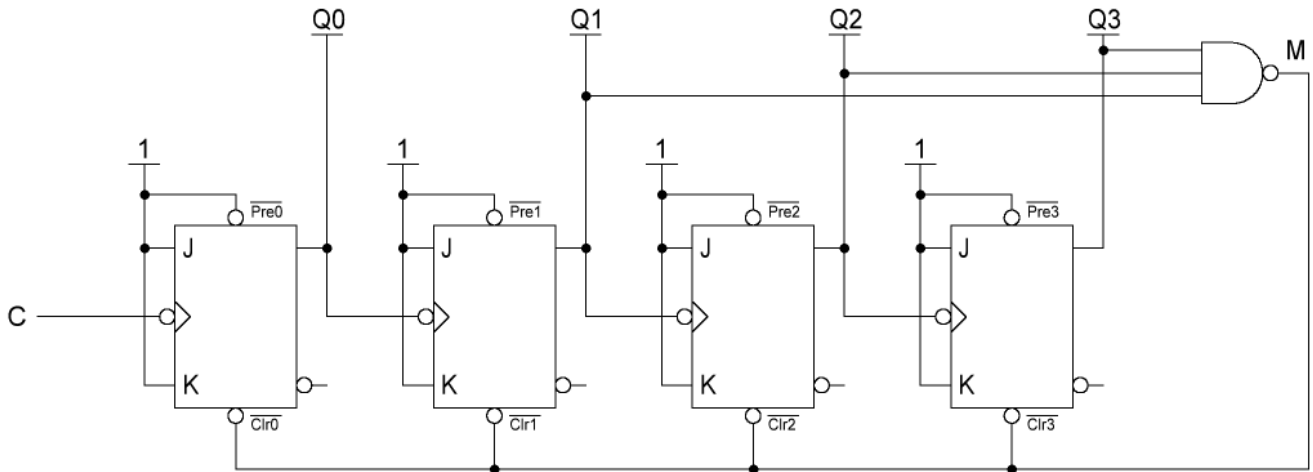


Figure 1


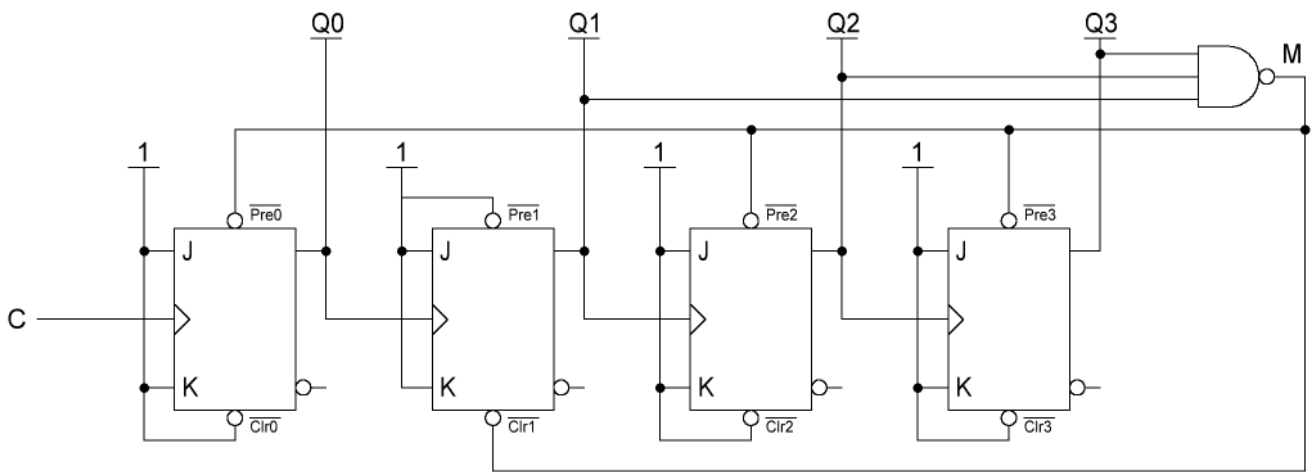


Figure 2

 

Exercise 4

Q2	Q1	Q0	J2	K2	J1	K1	J0	K0
1	1	1	Φ	0	Φ	1	Φ	1
1	0	0	Φ	0	0	Φ	1	Φ
1	0	1	Φ	0	1	Φ	Φ	1
1	1	0	Φ	1	Φ	0	0	Φ
0	1	0	0	Φ	Φ	1	1	Φ
0	0	1	0	Φ	0	Φ	Φ	1
0	0	0	1	Φ	1	Φ	1	Φ

Do not use Karnaugh maps for obvious solutions.

		Q1 Q0				
		J0	00	01	11	10
Q2	0	1	Φ	Φ	1	
	1	1	Φ	Φ	0	

$$J0 = \overline{Q2} + \overline{Q1}$$

		Q1 Q0				
		K0	00	01	11	10
Q2	0					
	1					

$$K0 = 1$$

		Q1 Q0				
		J1	00	01	11	10
Q2	0	1	0	Φ	Φ	
	1	0	1	Φ	Φ	

$$J1 = \overline{Q2} \cdot \overline{Q0} + Q2 \cdot Q0 = \overline{Q2} \oplus Q0$$

		Q1 Q0				
		K1	00	01	11	10
Q2	0	Φ	Φ	Φ	1	
	1	Φ	Φ	1	0	

$$K1 = \overline{Q2} + Q0$$


		Q1 Q0				
		J2	00	01	11	10
Q2	0	1	0	Φ	0	
	1	Φ	Φ	Φ	Φ	

$$J2 = \overline{Q1} \cdot \overline{Q0}$$

		Q1 Q0				
		K2	00	01	11	10
Q2	0	Φ	Φ	Φ	Φ	
	1	0	0	0	1	

$$K2 = Q1 \cdot \overline{Q0}$$

Feel free to use the blank space below if you need to:

 A large, empty rectangular box with a thin black border, occupying most of the page. It is intended for the student to write their answers to the exam questions.