

Final Exam S2

Computer Architecture

Duration: 1 hr 30 min

Answer on the answer sheet only.

Do not show any calculation unless you are explicitly asked.

Do not use a pencil or red ink.

Exercise 1 (5 points)

1. Convert the numbers given on the [answer sheet](#) into their **single-precision** IEEE-754 representations. Write down the final result in its **binary form** and specify the three fields.
2. Convert the **double-precision** IEEE-754 words given on the [answer sheet](#) into their associated representations. If a representation is a number, use the base-10 following form: $k \times 2^n$ where k and n are integers (either positive or negative).

Exercise 2 (5 points)

Answer the questions on the [answer sheet](#).

Exercise 3 (6 points)

The table shown on the [answer sheet](#) gives the sequence of a counter we want to design. This counter should be made up of JK flip-flops.

1. Complete the table shown on the [answer sheet](#).
2. Write down the most simplified expressions of J and K for each flip-flop on the [answer sheet](#). **Complete the Karnaugh maps for the solutions that are not obvious.** An obvious solution does not have any logical operations apart from the complement (for instance: $J_0 = 1$, $K_1 = \overline{Q_2}$).

Exercise 4 (2 points)

The table shown on the [answer sheet](#) gives the sequence of a counter we want to design. This counter should be made up of D flip-flops.

1. Complete the table shown on the [answer sheet](#).
2. Write down the most simplified expressions of D for each flip-flop on the [answer sheet](#). **Complete the Karnaugh maps for the solutions that are not obvious.** An obvious solution does not have any logical operations apart from the complement (for instance: $D_0 = 1$, $D_1 = \overline{Q_0}$).

Exercise 5 (2 points)

What are the two circuits below? Answer on the answer sheet.

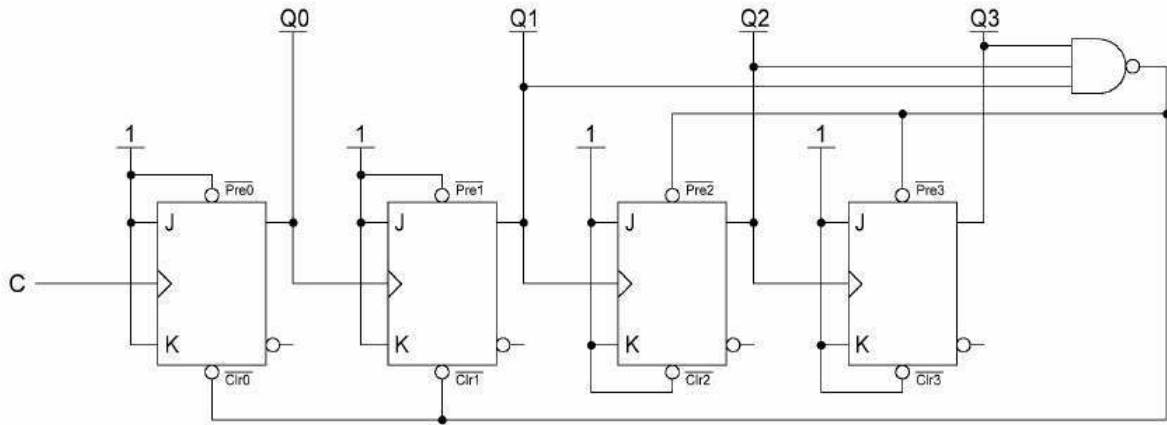


Figure 1

 


Figure 2

Last name: First name: Group:

ANSWER SHEET

Exercise 1

1.

Number	S	E	M
19.03125			
69×2^{-101}			

2.

IEEE-754 Representation	Associated Representation
4332000000000000_{16}	
2360000000000000_{16}	
$00EE000000000000_{16}$	

Exercise 2

Question	Answer
A memory has a depth of 32 Ki words. How many address lines does this memory have?	
A memory has a 16-bit data bus and a 16-bit address bus. In a power of two, what is the capacity in bits of this memory?	
An M1 memory has an 8-bit data bus and a 16-bit address bus. Two M1 memories are connected in series to build an M2 memory. What is the size of the address bus of the M2 memory?	
A microprocessor has a 24-bit address bus. Five address lines are used for selecting the devices. With the block address decoding, what is the maximum number of address lines that a device connected to this microprocessor can have?	
A microprocessor has a 20-bit address bus. Using the linear address decoding, we connect this microprocessor to the following devices. <ul style="list-style-type: none"> • a ROM device (15 address lines) • a RAM device (12 address lines) • a peripheral device (10 address lines) How many address lines are unused in the case of the RAM device?	

Exercise 3

Q2	Q1	Q0	J2	K2	J1	K1	J0	K0
0	0	0						
0	1	0						
1	0	0						
1	1	0						
0	0	1						
0	1	1						
1	0	1						
1	1	1						

Do not use Karnaugh maps for obvious solutions.

		Q1 Q0				
		J0	00	01	11	10
Q2	0					
	1					

J0 =

		Q1 Q0				
		K0	00	01	11	10
Q2	0					
	1					

K0 =

		Q1 Q0				
		J1	00	01	11	10
Q2	0					
	1					

J1 =

		Q1 Q0				
		K1	00	01	11	10
Q2	0					
	1					

K1 =

		Q1 Q0				
		J2	00	01	11	10
Q2	0					
	1					

J2 =

		Q1 Q0				
		K2	00	01	11	10
Q2	0					
	1					

K2 =

Exercise 4

Q1	Q0	D1	D0
0	0		
1	1		
0	1		
1	0		

Do not use Karnaugh maps for obvious solutions.

		Q0	
		0	1
Q1	D0		
	0		
1			

D0 =

		Q0	
		0	1
Q1	D1		
	0		
1			

D1 =

Exercise 5

Figure 1 :

Figure 2 :

Feel free to use the blank space below if you need to: