



Electronics Final Exam

Calculators and extra-documents are not allowed. The marking scale is given as a rough guide.

Please answer only on exam sheets. If more space is needed, write on the back.


Exercise 1. Rectifier with middle point (5 points)

Consider the following circuit:

The two sources v are exactly the same and $v(t) = V_M \sin(\omega t)$.

The diodes will be modelled by the ideal model.

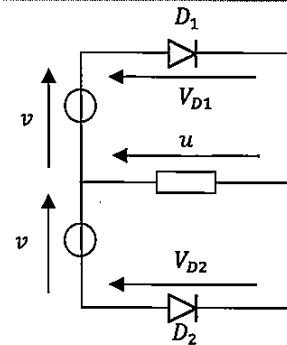- a) When the sources provide a positive voltage ($0 \leq t \leq \frac{T}{2}$), which diode is turned on? Justify your answer.




- b) Meanwhile, what is the expression of u ?


- c) When the sources provide a negative voltage ($\frac{T}{2} \leq t \leq T$), which diode is turned on? Justify your answer.

- d) Meanwhile, what is the expression of u ?

e) Draw $u(t)$.

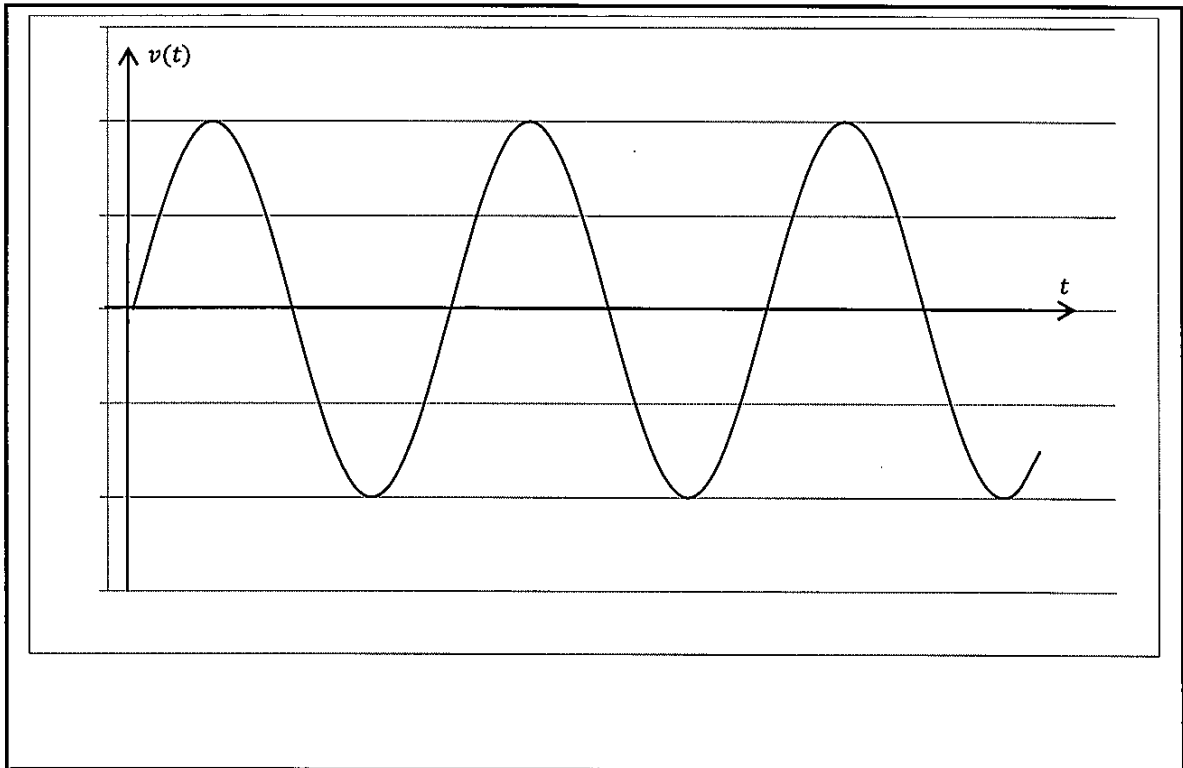

f) One now considers the threshold model for the diodes. Sketch the shape of $u(t)$, and justify your answer. We will denote V_0 the threshold voltage for each diode and we will assume that $V_M > V_0$.

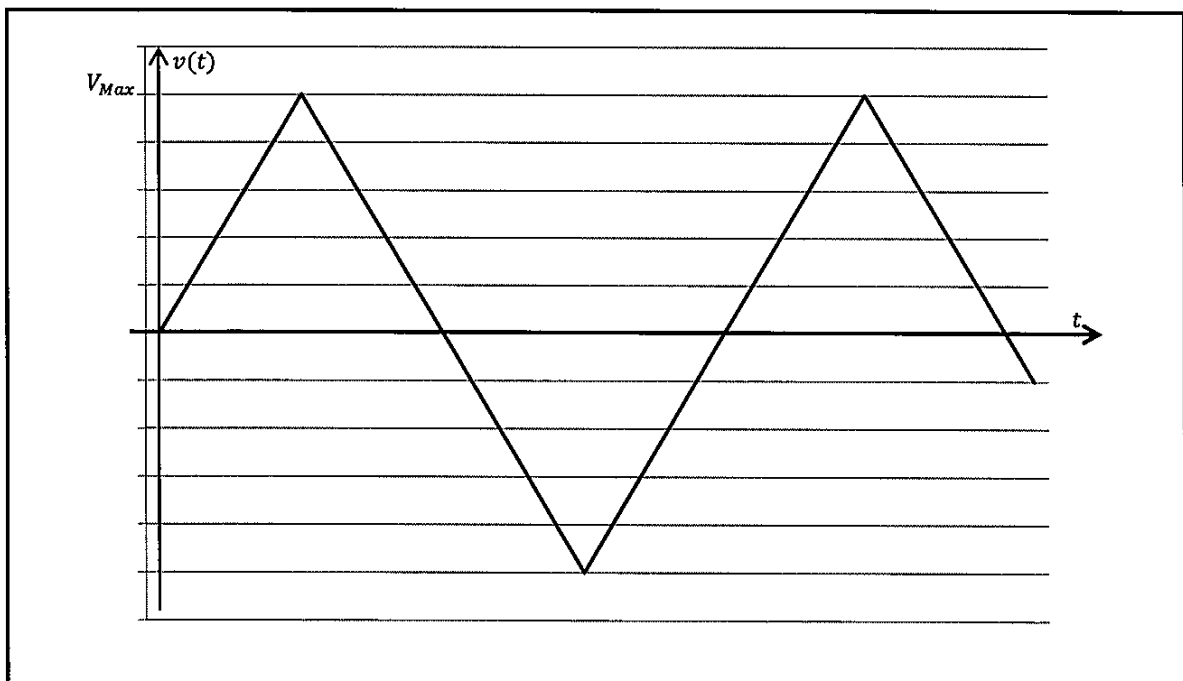


Exercise 2. Zéner's diode (4 points)

Consider the following diagram. $V \in \mathbb{R}$

Draw the transfer characteristic, namely $U = f(V)$. The diode will be replaced by its real model.

You will explicitly write the equations of each part of the characteristic. We will denote V_0 the threshold voltage, r_D the internal resistance of the diode for direct polarization, V_Z the Zéner threshold voltage and r_Z the internal resistance of the diode for reverse polarization.

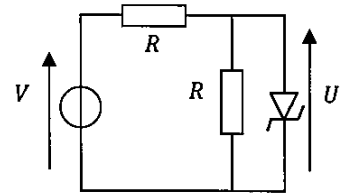

Exercise 3. Polarization (4 points)


Consider the following circuit.

Are given:

$$R_C = 4k\Omega, R_E = 1k\Omega, V_{CC} = 10V,$$

$$\beta = 100, V_{BE} = 0,6V \text{ if the junction Base-Emitter is turned on.}$$

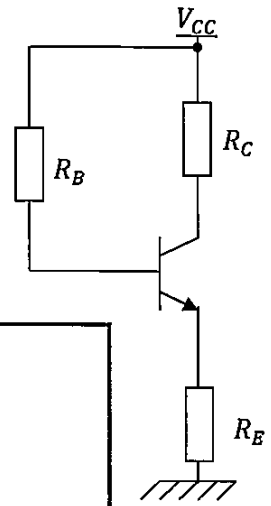1. Determine the saturation current $I_{C_{SAT}}$ of the transistor (which is the collector current when the transistor works in saturation regime).




2. Deduce the minimal value of the resistance R_B such that the transistor is linearly polarized in its working regime. We will consider that $\beta + 1 \approx \beta$.

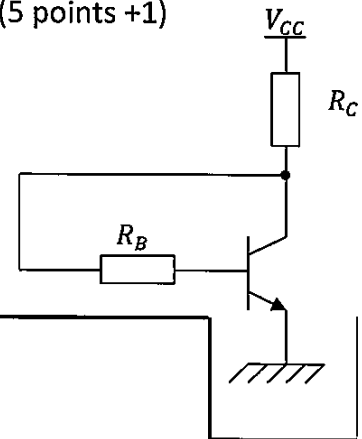Exercise 4. Polarization with back reaction to the collector (5 points +1)

Consider the following circuit:

Determine the polarization point of the transistor (namely the expressions of the currents I_B , I_C et I_E , and those of the voltages V_{BE} , V_{BC} et V_{CE}). Consider that $\beta + 1 \approx \beta$.



Bonus Question: By assuming that $V_{BE} = 0,7V$ if the junction Base-Emitter is turned on and that $V_{CE_{SAT}} = 0,2V$, can the transistor be saturated? Why? Remember that the transistor works in linear regime if $V_{CE} > V_{CE_{SAT}}$.

Exercise 5. MCQ (2 points – No negative point)

- Q1.** Doping increases the occurrence of thermogeneration.
 a- TRUE b- FALSE
- Q2.** If one takes some Silicon as semiconductor and then dopes it with Silicon, one gets:
 a- a N-Doping c- a NP-Doping
 b- a P-Doping d- no doping
- Q3.** In an intrinsic semiconductor, the number of free electrons is:
 a- equal to the hole number c- smaller than the hole number
 b- larger than the hole number d- none of the above
- Q4.** Consider the following circuit. Which type of logic gate does this circuit produce?
 a- AND c- NOT AND
 b- OR d- NOT OR

