



Electronics Midterm


The calculators and the extra-documents are not allowed. The marking scale is given as a rough guide.

Answer only on the exam sheet. If much space is needed, write on the back.

Exercise 1. Questions from class (MCQ without negative points – 5 points)

- Q1.** Material doping increases the conductivity of the semi-conductor.
- a- TRUE b- FALSE
- Q2.** The two kinds of doping are denoted by the letters P and N. What are they corresponding to?
- a- To the kind of ions injected in the semi-conductor.
b- These are the initials of the electronics engineers who discovered the semi-conductors.
c- To the polarity of the excess charge carriers.
d- None of the above.
- Q3.** We use the Silicium, which has 4 electrons in its valence band, as semi-conductor. If it is doped with Phosphorus, which has 5 electrons in its valence band, which kind of doping is realized?
- a- P-Doping c- NP-Doping
b- N-Doping d- No doping
- Q4.** A semi-conductor, which has a N-doping, is such that:
- a- its crystal structure lacks some electrons.
b- its crystal structure has too many electrons.
- Q5.** What is the roughest model of the diode:
- a- The ideal model c- The real model
b- The threshold model d- The three models are equivalent

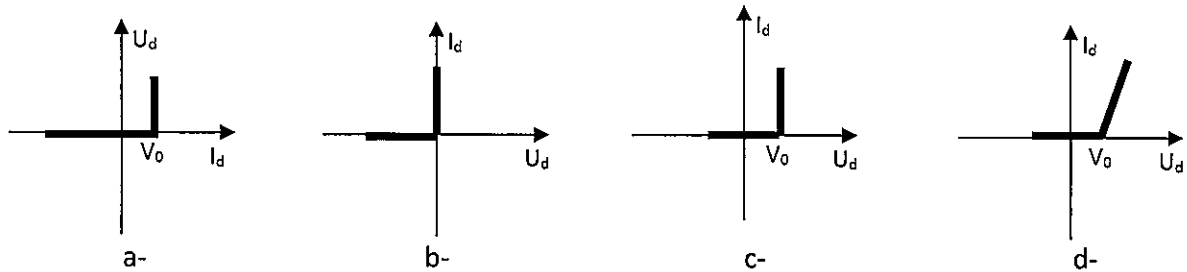Q6. Which characteristic corresponds to the current/voltage characteristic of the threshold model of the diode:



Q7. When a diode is turned off, it behaves as:

- a- A null resistance
- b- An open switch
- c- An ideal voltage generator
- d- A self


Q8. The dynamical resistance of a diode:

- a- has unit in Siemens.
- b- is the equivalent dipole of the diode when it is turned on.
- c- is usually very low.
- d- is usually huge.

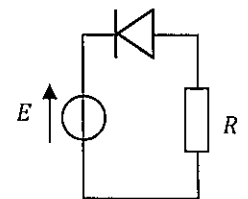Q9. Consider the following circuit. The diode D is ideal:

What is the value of the voltage of terminals of D if $E = 10V$, $R = 100\Omega$?


- a- $0V$
- b- $10V$
- c- $1kV$
- d- $0,1V$



Consider the following circuit:


Q10. Which kind of logic gates does this circuit realize?

- a- AND
- b- OR
- c- NAND
- d- NOR

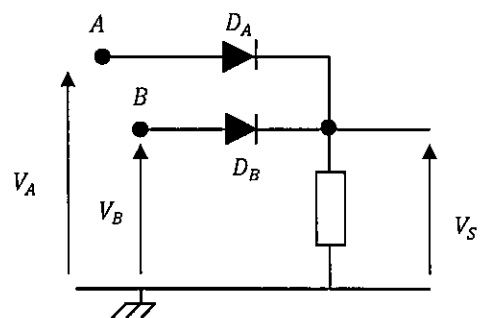


Exercise 2. SUP Review (4 points)

Consider the following circuit, where E_1, E_3, I_1, I_2 and R_i are known. The generators are independent. Determine the voltage U . You can choose any method that you prefer.

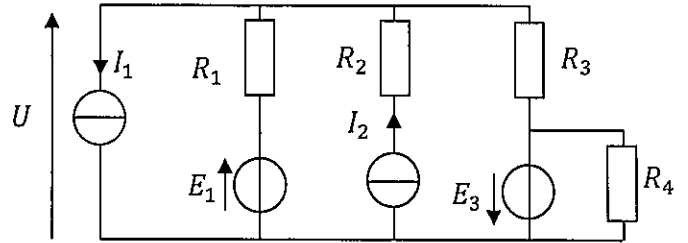

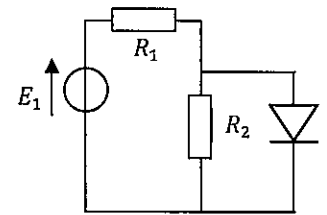Exercise 3. Diodes (5 points)

Consider the following circuit. The diode is modelled with its threshold model with $V_0 = 0,7V$. For the following questions, you will use a contradiction reasoning.



1. If $R_1 = 10k\Omega$, $R_2 = 10\Omega$ and $E = 10V$, prove that the diode is turned off. What is then the intensity of the current flowing through R_2 ?


2. If $R_1 = 50\Omega$, $R_2 = 100\Omega$ and $E = 10V$, prove that the diode is turned on. Determine then the intensity of the current flowing through it.

Exercise 4. Transfer characteristic (6 points)

Consider the following circuit:

We want to draw the characteristic $U = f(V)$.

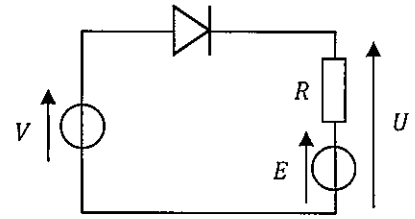The diode is modelled by its threshold model and its threshold voltage is denoted V_0 .




1. Give the expression of U if the diode is turned on.

2. Give the expression of U if the diode is turned off.

3. For which values of V is the diode turned off?

4. Draw $U = f(V)$.

 

5. Consider now that the voltage generator V generates a sinusoidal voltage $v(t) = V \cdot \sqrt{2} \cdot \sin(\omega t)$. Are given $V \cdot \sqrt{2} = 30 \text{ V}$, $E = 15 \text{ V}$ and $V_0 = 0,6 \text{ V}$. Draw the curve $u(t)$.

