



Electronics exam – Bipolar Transistors

[SI-S4-ELEC-2-TB]

Calculators and documents are forbidden. Scoring scale is given as a guide

Answers exclusively on the subject. If you need more space, you can use the back of the pages.


Exercise 1. MCQ (3 points – no negative score)

- Q1.** In active (or linear) mode, the base emitter junction operates in:
- Reverse mode
 - Direct mode
- Q2.** In saturation mode, the base emitter junction operates in:
- Reverse mode
 - Direct mode
- Q3.** In active mode (or linear):
- $I_B = \beta \cdot I_C$
 - $I_B > \frac{I_{C_{sat}}}{\beta}$
 - $V_{CE} > 0$
 - $V_{BC} = 0,6V$


Q4. In active mode, what is the correct relation between these intensities:

- $I_B + I_C + I_E = 0$
- $I_B = I_C + I_E$
- $I_B + I_C = I_E$
- Node's law depends on the transistor type, therefore, none of the laws above can be applied both for NPN and PNP transistors.

Transistor npn

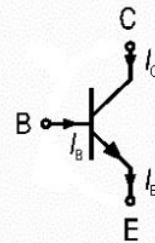

Transistor pnp

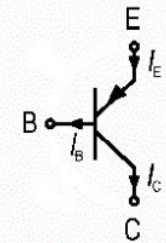

Q5. When a NPN bipolar transistor operates in saturation mode, then: (1 or more correct choices)


- No current is flowing through the transistor
- The transistor behaves like a closed switch between the collector and the emitter.
- The transistor behaves like an open switch between the collector and the emitter.
- The collector current reaches the maximum value fixed by the circuit (i.e. power supplies, resistors...)

Q6. Cutoff and saturation modes of a bipolar transistor are used to design logic gates

- TRUE
- FALSE

Exercise 2. Amplifier (10 points)

Consider the diagram below:

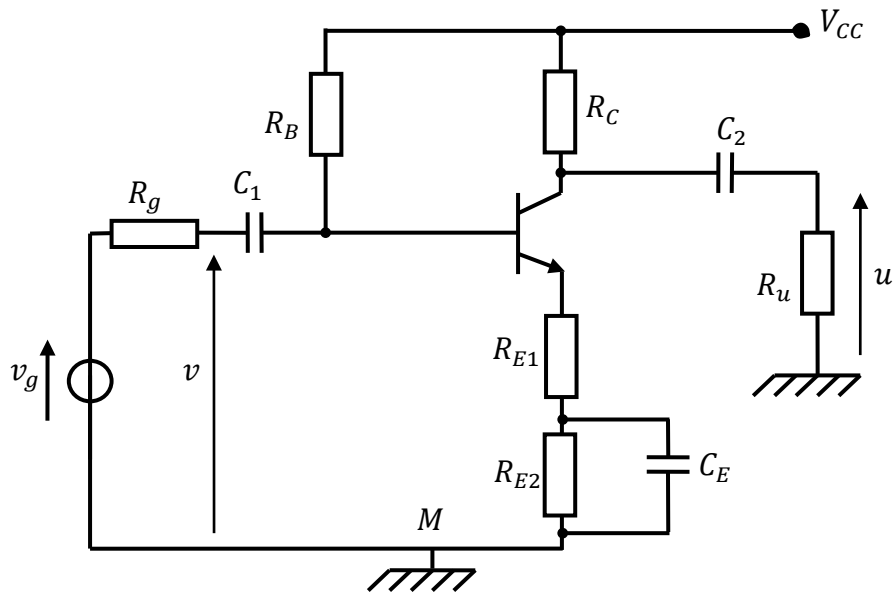

Capacitors C_1 and C_2 are called « link capacitors ». Capacitor C_E is a decoupling capacitor.

We set:

$$R_B = 150k\Omega, R_C = 1k\Omega, R_{E1} = 500\Omega, R_{E2} = 1k\Omega, V_{CC} = 10V, V_{BE} = 0,7V \text{ et } \beta = 100.$$

A. Bias study (DC signals)

1. Draw the bias scheme.

- Determine the currents I_B and I_C as well as the voltage V_{CE} . We assume the transistor operating in active mode (no need to justify the operation mode) and that $1 + \beta \approx \beta$.




B. Small signal study (AC signals)

- Draw the small signal equivalent scheme from the diagram above.



2. Determine the expression of voltage amplification A_v . (We assume $1 + \beta \approx \beta$ and we neglect the transistor output resistance r_o) – (give the expression of v and u in terms of i_b .)

 


Exercise 3. Darlington setup (2 points)

Consider the diagram on the opposite.

β_1 is the transfer coefficient of the base current (also called Current gain) of the transistor on the left and β_2 represents the same coefficient for the transistor on the right. Determine the current gain β of the transistor equivalent to this association, in terms of β_1 and β_2 .

We assume both transistors operating in active mode (no need to justify it!).

Indication: Determine I_C in terms of I_B .

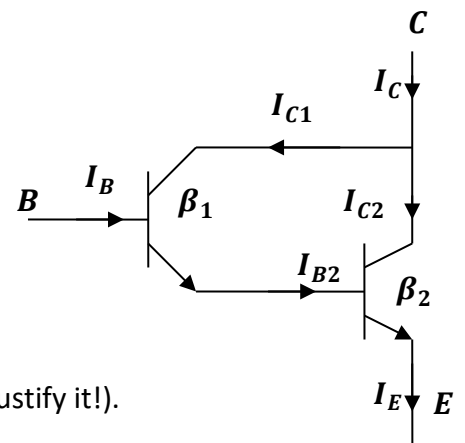


Exercise 4. Polarization (bias) by feedback to the collector (5 points)

Consider the scheme on the opposite where the transistor operates in active mode:

Determine the polarization (bias) point of the transistor (i.e. the expressions of the currents I_B , I_C and I_E , as well as the voltages V_{BC} and V_{CE} . Express your results in terms of V_{CC} , R_C , R_B et, V_{BE}).

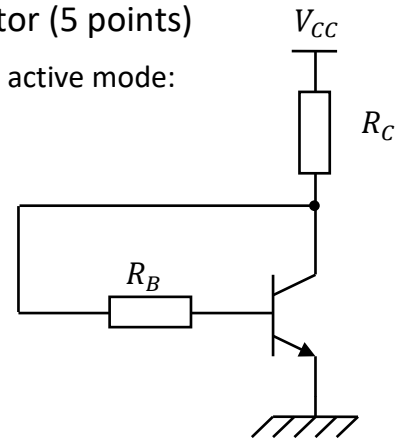We assume $\beta + 1 \approx \beta$ and $V_{BE} = 0,7V$.



A large empty rectangular box provided for the student to write their solution to the exercise.